

CSE 502:

Computer Architecture

SystemVerilog

More Resources

- Cannot cover everything in one day
- You will likely need to look up reference material:
 - SystemVerilog for VHDL Users:
http://www.systemverilog.org/techpapers/date04_systemverilog.pdf
 - <http://www.doulos.com/knowhow/sysverilog/>
 - http://www.eda.org/sv/SystemVerilog_3.1a.pdf
 - <http://electrosofts.com/systemverilog/operators.html>
 - <http://www.cl.cam.ac.uk/teaching/1011/ECAD+Arch/files/SystemVerilogCheatSheet.pdf>
 - http://www.sunburst-design.com/papers/CummingsSNUG2003SJ_SystemVerilogFSM.pdf

Basic Module Setup

- Assume:
 - a, b, c are inputs to module
 - f is output of module
 - module is named “mymodule”

declare which
ports are inputs,
which are outputs

```
module mymodule(a, b, c, f);  
    output f;  
    input a, b, c;  
  
    // Description goes here  
  
endmodule
```

all ports declared here


Module Instantiation

- Just like C++ object instantiation
 - Module name is analogous to Class name
 - Inputs/outputs are analogous to constructor arguments

```
module mymodule(a, b, c, f);  
    output f;  
    input a, b, c;  
  
    module_name instance_name(port_connections);  
endmodule
```

Structural Design

 - Example: multiplexor
 - Output equals an input
 - Which one depends on “sel”



datatype for describing logical value

instantiate gates as above

```

module mux(a, b, sel, f);
    output f;
    input a, b, sel;

    logic c, d, not_sel;

    not gate0(not_sel, sel);
    and gate1(c, a, not_sel);
    and gate2(d, b, sel);
    or gate3(f, c, d);
endmodule
    
```


Continuous Assign Statement

- Specify behavior with assign statement and bit ops.

```

module mux2(a, b, sel, f);
    output f;
    input a, b, sel;
    logic c, d;

    assign c = a & (~sel);
    assign d = b & sel;
    assign f = c | d;
endmodule
    
```

 

Procedural Statement

- Can specify behavior of combinational logic procedurally using `always_comb` block

```
module mymodule(a, b, c, f);
    output f;
    input a, b, c;

    always_comb begin
        // Combinational logic described in
        // C-like syntax
    end
endmodule
```

Procedural Behavioral Mux Description

```
module mux3(a, b, sel, f);  
  output logic f;  
  input a, b, sel;  
  
  always_comb begin  
    if (sel == 0) begin  
      f = a;  
    end  
    else begin  
      f = b;  
    end  
  end  
end  
endmodule
```

If we are going to drive f this way, need to declare it as logic

Important: for behavior to be combinational, every output (f) must be assigned in all possible control paths

Why? Otherwise, would be a latch

Condensed if-then-else Form

- Syntax borrowed from C:

```
if (a)
    b = c;
else
    b = d;
```

same as

```
b = (a) ? c : d;
```

- So, we can simplify the mux:

```
...
always_comb begin
    f = (sel) ? b : a;
end
...
```

- Or even skip the always_comb block:

```
assign f = (sel) ? b : a;
```

Accidental Latch Description

```
module bad(a, b, f);
    output logic f;
    input a, b;

    always_comb begin
        if (b == 1) begin
            f = a;
        end
    end
endmodule
```

- This is not combinational, because for certain values of b, f must **remember** its previous value.
- This code describes a latch. (If you want a latch, you should define it using `always_latch`)

Don't do this!

Multiply-Assigned Values

```
module bad2 (...);  
    ...  
  
    always_comb begin  
        b = ... something ...  
    end  
  
    always_comb begin  
        b = ... something else ...  
    end  
  
endmodule
```

- Both of these blocks execute ***concurrently***
- So what is the value of b?
We don't know!

Don't do this!

Multi-Bit Values

- Can define inputs, outputs, or logic with multiple bits

```
module mux4(a, b, sel, f);
    output logic [3:0] f;
    input [3:0] a, b;
    input sel;

    always_comb begin
        if (sel == 0) begin
            f = a;
        end
        else begin
            f = b;
        end
    end
endmodule
```

Multi-Bit Constants and Concatenation

- Can give constants with specified number bits
 - In binary or hexadecimal
- Can concatenate with { and }
- Can reverse order (to index buffers left-to-right)

```
logic [3:0] a, b, c;
logic signed [3:0] d;
logic [1:0] e, f;
assign a = 4'b0010; // four bits, specified in binary
assign b = 4'hC; // four bits, specified in hex == 1100
assign c = 3; // == 0011
assign d = -2; // 2's complement == 1110 as bits
assign e = {a, b}; // concatenate == 0010_1100
assign f = a[2 : 1]; // two bits from middle == 01
assign g = b[c +: 2]; // two bits from bit c == 11
```

Case Statements and “Don’t-Cares”

```
module newmod(out, in0, in1, in2);
  input in0, in1, in2;
  output logic out;

  always_comb begin
    case({in0, in1, in2})
      3'b000: out = 1;
      3'b001: out = 0;
      3'b010: out = 0;
      3'b011: out = x;
      3'b10x: out = 1;
      default: out = 0;
    endcase
  end
endmodule
```

output value is
undefined in this case

Last bit is a “don’t
care” -- this line will
be active for 100 OR
101

default gives “else”
behavior. Here active
if 110 or 111

Arithmetic Operators

- Standard arithmetic operators defined: + - * / %
- Many subtleties here, so be careful:
 - four bit number + four bit number = five bit number
 - Or just the bottom four bits
 - arbitrary division is difficult

Addition and Subtraction

- Be wary of overflow!

```
logic [3:0] d, e, f;
assign f = d + e;
```

$4'b1000 + 4'b1000 = \dots$
In this case, overflows to zero

```
logic [3:0] a, b;
logic [4:0] c;
assign c = a+b;
```

Five bit output can prevent overflow:
 $4'b1000 + 4'b1000$ gives $5'b10000$

- Use “signed” if you want values as 2’s complement

$i == 4'b1010 == -6$
 $j == 5'b11010 == -6$

```
logic signed [3:0] g, h, i;
logic signed [4:0] j;
assign g = 4'b0001; // == 1
assign h = 4'b0111; // == 7
assign i = g - h;
assign j = g - h;
```



Multiplication

- Multiply k bit number with m bit number
 - How many bits does the result have?

```
logic signed [3:0] a, b;  
logic signed [7:0] c;  
assign a = 4'b1110; // -2  
assign b = 4'b0111; // 7  
assign c = a*b;
```

$k+m$

$c = 8'b1111_0010 == -14$

- If you use fewer bits in your code
 - Get least significant bits of the product

```
logic signed [3:0] a, b, d;  
assign a = 4'b1110; // -2  
assign b = 4'b0111; // 7  
assign d = a*b;
```

$d = 4'0010 == 2$

Underflow!

Sequential Design

- Everything so far was purely combinational
 - Stateless
- What about *sequential* systems?
 - flip-flops, registers, finite state machines
- New constructs
 - `always_ff @ (posedge clk, ...)`
 - non-blocking assignment `<=`

Edge-Triggered Events

- Variant of `always` block called `always_ff`
 - Indicates that block will be sequential logic (flip flops)
- Procedural block occurs only on a signal's edge
 - `@ (posedge ...)` or `@ (negedge ...)`

```
always_ff @(posedge clk, negedge reset_n) begin

    // This procedure will be executed
    // anytime clk goes from 0 to 1
    // or anytime reset_n goes from 1 to 0

end
```

Flip Flops (1/3)

- q remembers what d was at the last clock edge
 - One bit of memory
- Without reset:

```
module flipflop(d, q, clk);  
    input d, clk;  
    output logic q;  
  
    always_ff @(posedge clk) begin  
        q <= d;  
    end  
endmodule
```

Flip Flops (2/3)

- Asynchronous reset:

```
module flipflop_asyncr(d, q, clk, rst_n);
  input d, clk, rst_n;
  output logic q;

  always_ff @(posedge clk, negedge rst_n) begin
    if (rst_n == 0)
      q <= 0;
    else
      q <= d;
  end
endmodule
```

Flip Flops (3/3)

- Synchronous reset:

```
module flipflop_syncr(d, q, clk, rst_n);
    input d, clk, rst_n;
    output logic q;

    always_ff @(posedge clk) begin
        if (rst_n == 0)
            q <= 0;
        else
            q <= d;
        end
    endmodule
```

Multi-Bit Flip Flop

```
module flipflop_asyncr(d, q, clk, rst_n);
    input [15:0] d;
    input clk, rst_n;
    output logic [15:0] q;

    always_ff @(posedge clk, negedge rst_n) begin
        if (rst_n == 0)
            q <= 0;
        else
            q <= d;
        end
    endmodule
```

Parameters

- Parameters allow modules to be easily changed

```
module my_flipflop(d, q, clk, rst_n);  
    parameter WIDTH=16;  
    input [WIDTH-1:0] d;  
    input clk, rst_n;  
    output logic [WIDTH-1:0] q;  
  
    ...  
endmodule
```

default value set to 16

- Instantiate and set parameter:

```
my_flipflop f0(d, q, clk, rst_n);
```

uses default value

```
my_flipflop #(12) f0(d, q, clk, rst_n);
```

changes parameter to 12 for this instance


Non-Blocking Assignment $a \leq b$;

- \leq is the non-blocking assignment operator
 - All left-hand side values take new values concurrently

```
always_ff @(posedge clk) begin
    b <= a;
    c <= b;
end
```

c gets the **old** value of b, not value assigned just above

- This models synchronous logic!

 

Non-Blocking vs. Blocking

- Use non-blocking assignment `<=` to describe edge-triggered (synchronous) assignments

```
always_ff @(posedge clk) begin
    b <= a;
    c <= b;
end
```

- Use blocking assignment `=` to describe combinational assignment


```
always_comb begin
    b = a;
    c = b;
end
```

Design Example

- Let's say we want to compute $f = a + b * c$
 - b and c are 4 bits, a is 8 bits, and f is 9 bits
- First, we will build it as a combinational circuit
- Then, we will add registers at its inputs and outputs


Finite State Machines (1/2)

 - State names
- Output values
- Transition values
- Reset state



Finite State Machines (2/2)

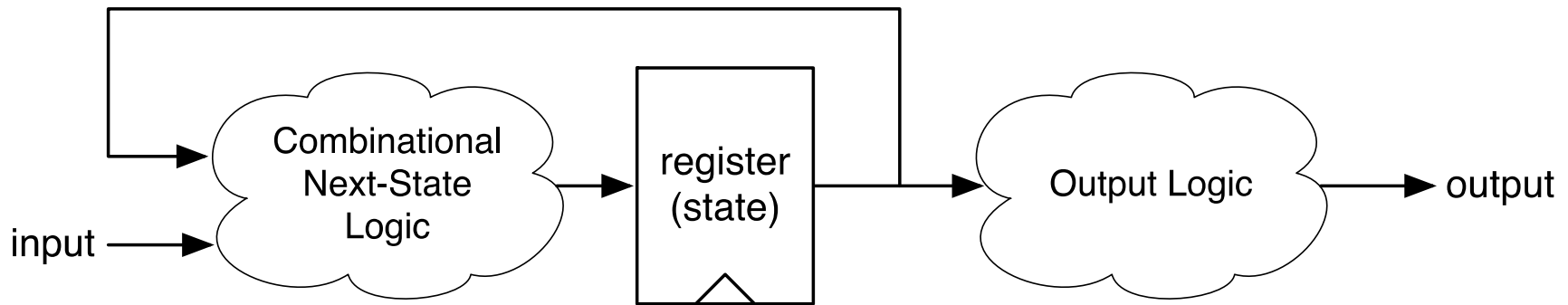- What does an FSM look like when implemented?



- Combinational logic and registers
(things we already know how to do!)

Full FSM Example (1/2)

```
module fsm(clk, rst, x, y);
    input clk, rst, x;
    output logic [1:0] y;
    enum { STATEA=2'b00, STATEB=2'b01, STATEC=2'b10,
          STATED=2'b11 } state, next_state;

    // next state logic
    always_comb begin
        case(state)
            STATEA: next_state = x ? STATEB : STATEA;
            STATEB: next_state = x ? STATEC : STATED;
            STATEC: next_state = x ? STATED : STATEA;
            STATED: next_state = x ? STATEC : STATEB;
        endcase
    end

    // ... continued on next slide
end
```

Full FSM Example (2/2)

```
// ... continued from previous slide
// register
always_ff @(posedge clk) begin
    if (rst)
        state <= STATEA;
    else
        state <= next_state;
end
always_comb begin // Output logic
    case(state)
        STATEA: y = 2'b00;
        STATEB: y = 2'b00;
        STATEC: y = 2'b11;
        STATED: y = 2'b10;
    endcase
end
endmodule
```

Multi-Dimensional Arrays

```
module multidimarraytest();
    logic [2:0][3:0] myarray;

    assign myarray[0] = 4'b0010;
    assign myarray[1][3:2] = 2'b01;
    assign myarray[1][1] = 1'b1;
    assign myarray[1][0] = 1'b0;
    assign myarray[2][3:0] = 4'hC;
    initial begin
        $display("myarray == %b", myarray);
        $display("myarray[2:0] == %b", myarray[2:0]);
        $display("myarray[1:0] == %b", myarray[1:0]);
        $display("myarray[1] == %b", myarray[1]);
        $display("myarray[1][2] == %b", myarray[1][2]);
        $display("myarray[2][1:0] == %b", myarray[2][1:0]);
    end
endmodule
```


Memory (Combinational read)

```
module mymemory(clk, data_in, data_out,
                r_addr, w_addr, wr_en);
    parameter WIDTH=16, SIZE=256, LOGSIZE=8;
    input  [WIDTH-1:0] data_in;
    output logic [WIDTH-1:0] data_out;
    input  clk, wr_en;
    input  [LOGSIZE-1:0] r_addr, w_addr;

    logic [SIZE-1:0][WIDTH-1:0] mem;

    assign data_out = mem[r_addr];

    always_ff @(posedge clk) begin
        mem <= mem;
        if (wr_en)
            mem[w_addr] <= data_in;
    end
endmodule
```

Combinational read

Default: memory does not
change

Synchronous write

Memory (Synchronous read)

```
module mymemory2(clk, data_in, data_out,
                 r_addr, w_addr, wr_en);
    parameter WIDTH=16, SIZE=256, LOGSIZE=8;
    input  [WIDTH-1:0] data_in;
    output logic [WIDTH-1:0] data_out;
    input  clk, wr_en;
    input  [LOGSIZE-1:0] r_addr, w_addr;

    logic [SIZE-1:0][WIDTH-1:0] mem;

    always_ff @(posedge clk) begin
        data_out <= mem[r_addr];

        mem <= mem;
        if (wr_en)
            mem[w_addr] <= data_in;
    end
endmodule
```

Synchronous read


What happens if we try to read and write the same address?

Assertions

- Assertions are test constructs
 - Automatically validated as design as simulated
 - Written for properties that must always be true
- Makes it easier to test designs
 - Don't have to manually check for these conditions

 Example: A good place for assertions

- Imagine you have a FIFO queue
 - When queue is full, it sets `status_full` to true
 - When queue is empty, it sets `status_empty` to true



- When `status_full` is true, `wr_en` must be false
- When `status_empty` is true, `rd_en` must be false

Immediate Assertions

- Checks an expression when statement is executed

```
assertion_name: assert(expression)
    pass_code;
else
    fail_code;
```

- Example:

```
always @(posedge clk) begin
    assert((status_full == 0) || (wr_en == 0))
    else $error("Tried to write to FIFO when full.");
end
```

Use `$display` to print text, or `$error` to print an error message, or `$fatal` to print an error message and halt simulation